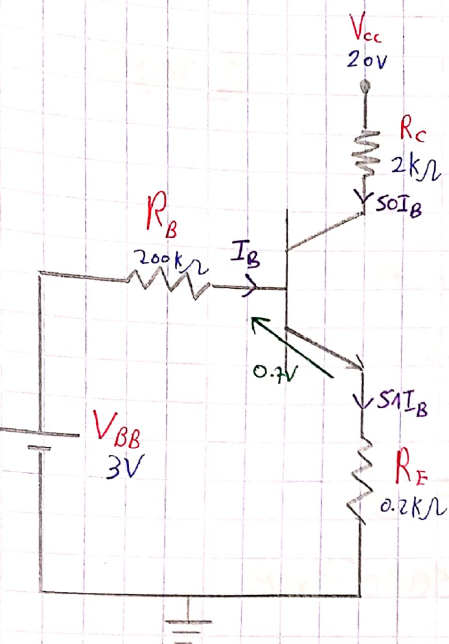




1. חישוב

1. חישוב

$$V_{BB} - 0 = U_{RB} + V_{BE} + U_{RE}$$

$$3 = 200 I_B + 0.7 + 51 I_B \cdot 0.2$$

$$I_B = 10.941 \cdot 10^{-3} \text{ mA}$$


$$I_C = 50 I_B = 0.547 \text{ mA}$$

2. חישוב


$$V_{CC} - 0 = U_{RC} + V_{CE} + U_{RE}$$

$$20 = 50 I_B \cdot 2 + V_{CE} + 51 I_B \cdot 0.2$$

$$V_{CE} = 18.794 \text{ V}$$

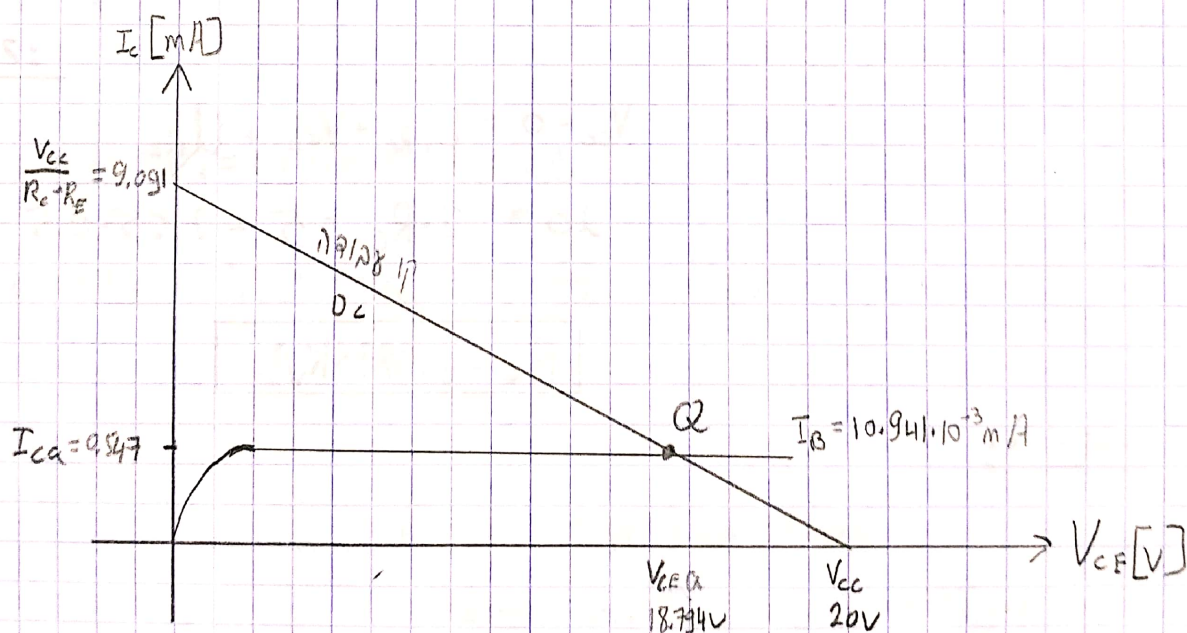

חישוב נקודת המנוחה

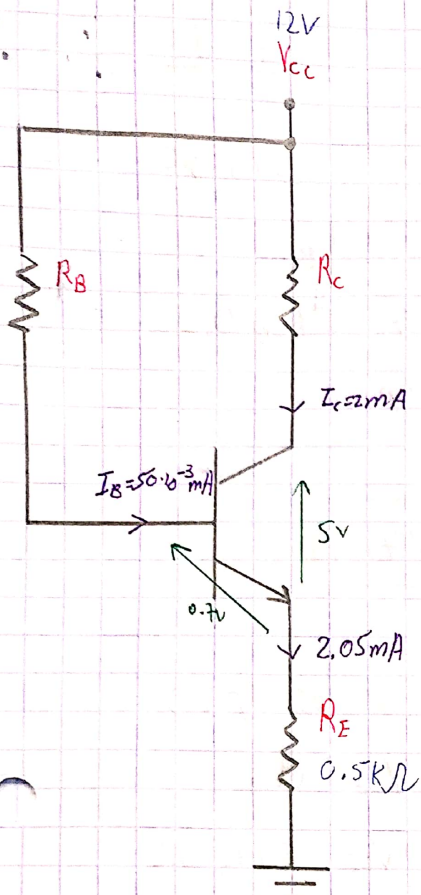

2. 2.10

$$\beta = 40$$

$$I_C = 2 \text{ mA}$$

$$I_C = \beta I_B$$

↓

$$2 = 40 I_B$$

$$I_B = 50 \cdot 10^{-3} \text{ mA}$$

$$V_{CC} - 0 = U_{RB} + V_{BE} + U_{RE} \quad : 1. \text{ 2.10}$$

$$20 = 50 \cdot 10^{-3} \cdot R_B + 0.7 + 2.05 \cdot 0.5$$



$$R_B = 365.5 \text{ k}\Omega$$

: 2. 2.10

$$V_{CC} - 0 = U_{RC} + V_{CE} + U_{RE}$$

$$20 = 2 \cdot R_C + 5 + 2.05 \cdot 0.5$$

$$R_C = 6.9875 \text{ k}\Omega$$

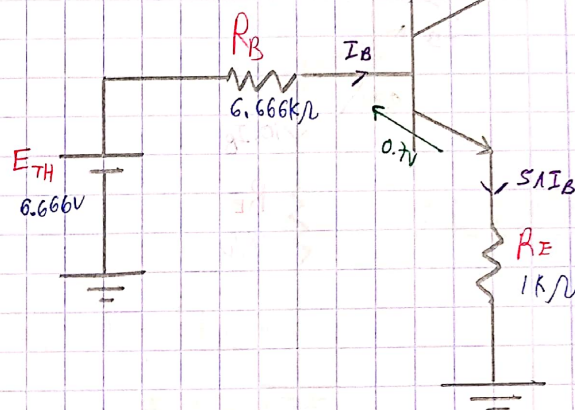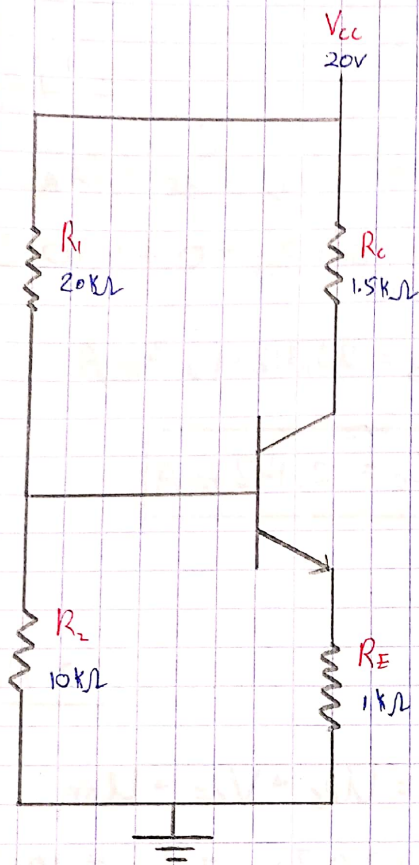

$$R_{TH} = R_2 \parallel R_1 = 10 \parallel 20 = 6.666k\Omega$$

$$E_{TH} = U_{R2} = V_{CC} \cdot \frac{R_2}{R_2 + R_1} = 20 \cdot \frac{10}{30} = 6.666V$$

1.10

$$E_{TH} - 0 = U_{RB} + V_{BE} + U_{RE}$$

$$6.666 = 6.666 I_B \cdot 0.7 + 51 I_B \cdot 1$$

$$I_B = 103.468 \cdot 10^{-3} \text{ mA}$$




$$I_C = 5.173 \text{ mA}$$

2.10

$$V_{CC} - 0 = U_{RC} + V_{CE} + U_{RE}$$

$$20 = 50 I_B \cdot 1.5 + V_{CE} + 51 I_B \cdot 1$$

$$V_{CE} = 6.963 \text{ V}$$

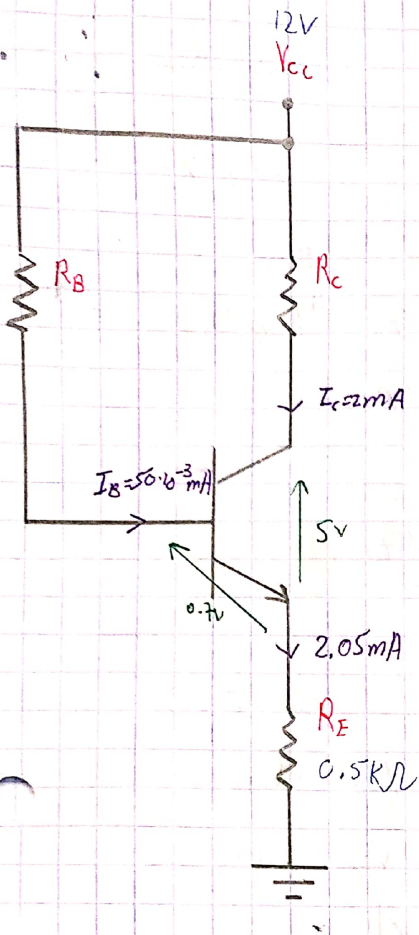

2. 20V

$$\beta = 40$$

$$I_C = 2mA$$

$$I_C = \beta I_B$$

↓

$$2 = 40 I_B$$

$$I_B = 50 \cdot 10^{-3} mA$$

$$V_{cc} - 0 = U_{RB} + V_{BE} + U_{RE} \quad : 1 \text{ p. 10}$$

$$20 = 50 \cdot 10^{-3} \cdot R_B + 0.7 + 2.05 \cdot 0.5$$


$$R_B = 365.5 k\Omega$$

: 2 p. 10

$$V_{cc} - 0 = U_{RC} + V_{CE} + U_{RE}$$

$$20 = 2 \cdot R_C + 5 + 2.05 \cdot 0.5$$

$$R_C = 6.9875 k\Omega$$

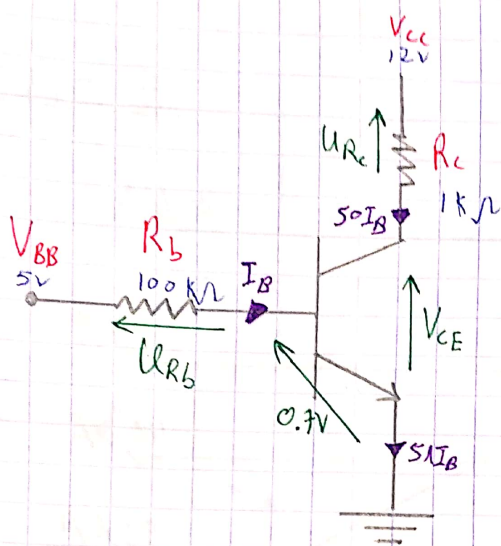

5. Aufgabe

: 1. Teil

$$V_{BB} - 0 = U_{RB} + V_{BE}$$

$$5 = 100 I_B + 0.7$$

$$I_B = 43 \cdot 10^{-3} \text{ mA}$$



$$I_C = 50 I_B = 2.15 \text{ mA}$$

: 2. Teil

$$V_{CC} - 0 = U_{RC} + V_{CE}$$

$$12 = 50 I_B \cdot 1 + V_{CE}$$

$$V_{CE} = 9.85 \text{ V}$$

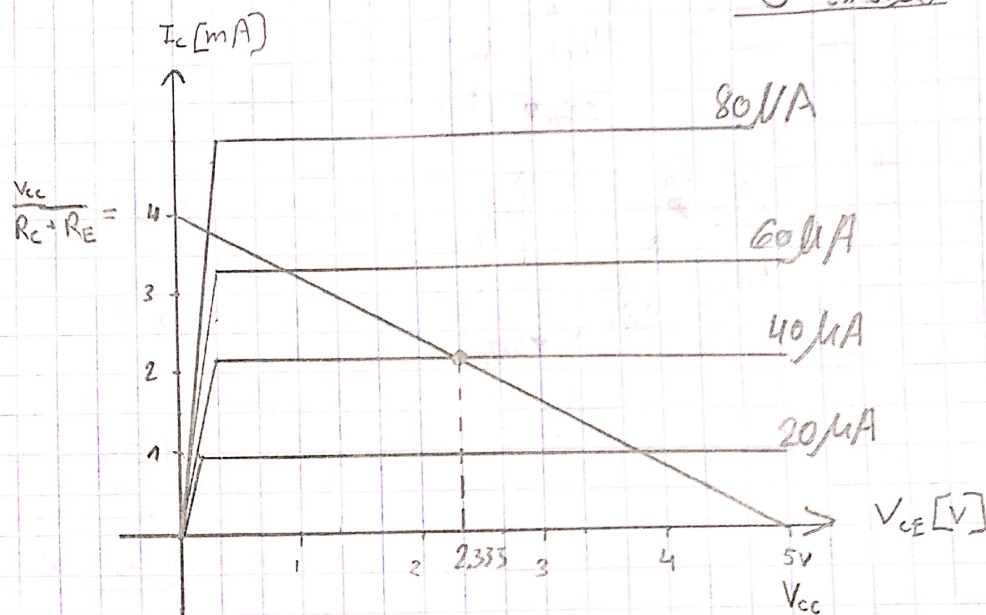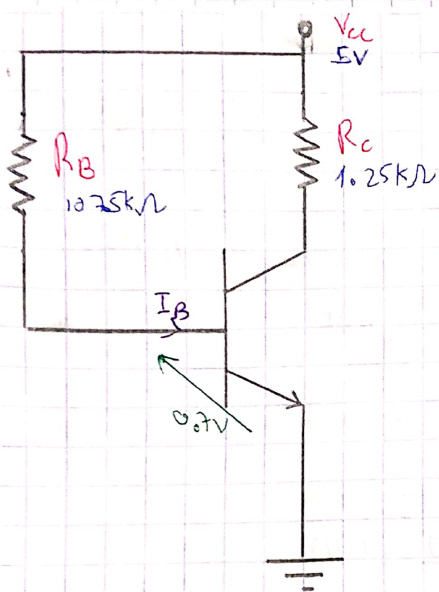



$$V_{CC} - 0 = I_{RB} + V_{BE}$$

$$5 = 107.5 I_B + 0.7$$

$$I_B = 0.04 \text{ mA}$$

$$I_B = 40 \cdot 10^{-3} \text{ mA}$$

$$V_{CE} = 2.333 \text{ V}$$

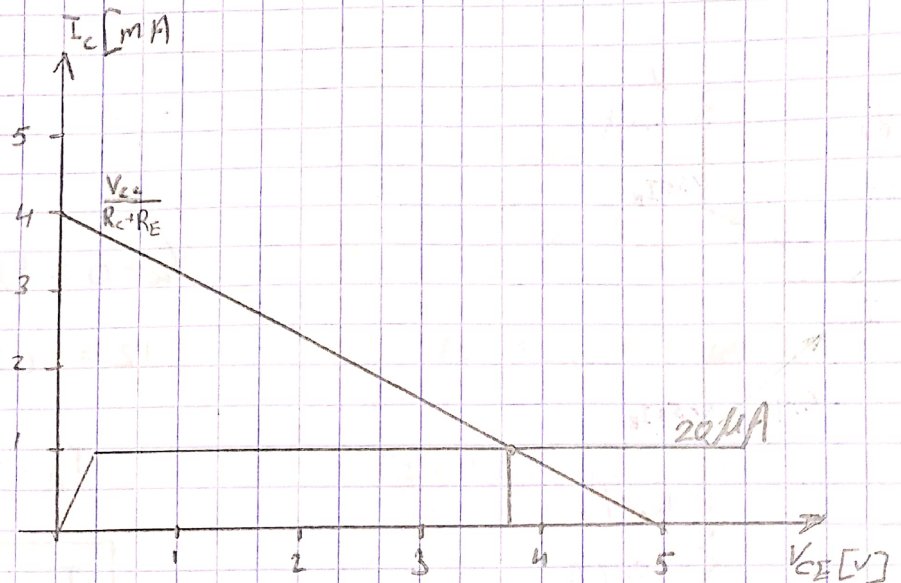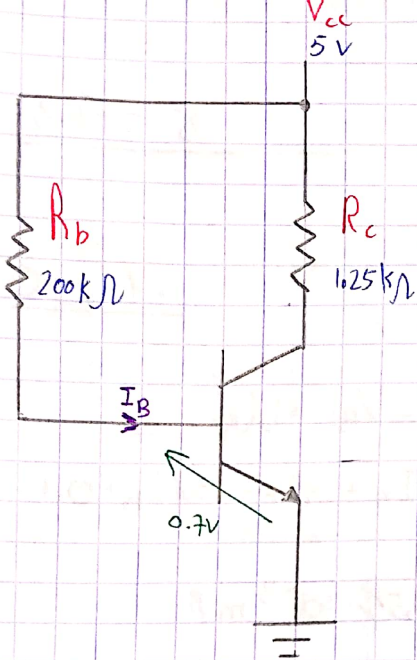

המיקוד

$$V_{cc} - 0 = U_{RB} + V_{BE}$$

$$5 = 200 I_B + 0.7$$

$$I_B = 21.5 \cdot 10^{-3} \text{ mA} \approx 20 \cdot 10^{-3} \text{ mA}$$

$$V_{CE} = 3.7 \text{ V}$$

ה

לפי V_{CE} ו- V_{CE} שיתר קרוב $\frac{1}{2} V_{cc}$


לכן הפיתרון כאן 6 יותר קרוב

כי כך נוסח הערך יותר קרוב

הערות נוספות

שאלה 8

סעיף 1:

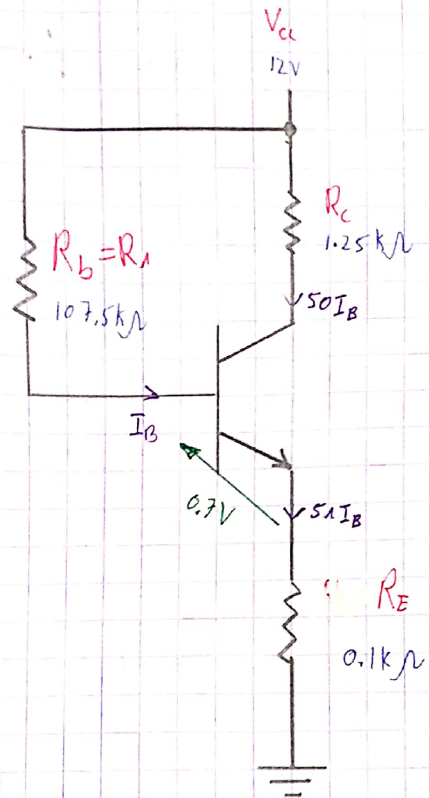

$$V_{cc} - 0 = U_{Rb} + V_{BE} + U_{RE}$$

$$12 = 107.5 I_B + 0.7 + 51 I_B \cdot 0.1$$

$$I_B = 100.355 \cdot 10^{-3} \text{ mA}$$

$$I_C = 5.017 \text{ mA}$$

סעיף 2:

$$V_{cc} - 0 = U_{Rc} + V_{CE} + U_{RE}$$

$$12 = 1.25 \cdot 50 \cdot I_B + V_{CE} + 0.1 \cdot 51 \cdot I_B$$

$$V_{CE} = 5.215 \text{ V}$$

ב. מתקשר המא: (סעיף 2)

$$12 - 1.25 \cdot 50 I_B - 0.1 \cdot 51 \cdot I_B = V_{CE}$$

המורה והיציב של המעגל (יחס הסף) - מתקשר סעיף 1

כאשר V_{CE} הוא מתח המעגל, I_B הוא זרם הבסיס, ו- R_B/R_A הוא יחס ההתחלקות.

$$I_B (5.1 + R_A) = 11.3$$

$$88.757 \cdot 10^{-3} (5.1 + R_A) = 11.3$$

$$R_A = 122.213 \text{ k}\Omega$$

סעיף 2:

$$V_{cc} - 0 = U_{Rc} + V_{CE} + U_{RE}$$

$$12 = 50 \cdot I_B \cdot 1.25 + 6 + 51 I_B \cdot 0.1$$

$$I_B (62.5 + 5.1) = 6$$

$$67.6 \cdot I_B = 6$$

$$I_B = 88.757 \cdot 10^{-3} \text{ mA}$$


סעיף 1:

$$V_{cc} - 0 = U_{Rb} + V_{BE} + U_{RE}$$

$$12 = R_A \cdot I_B + 0.7 + 0.1 \cdot 51 I_B$$

$$I_B (5.1 + R_A) = 11.3$$

ג' חלק

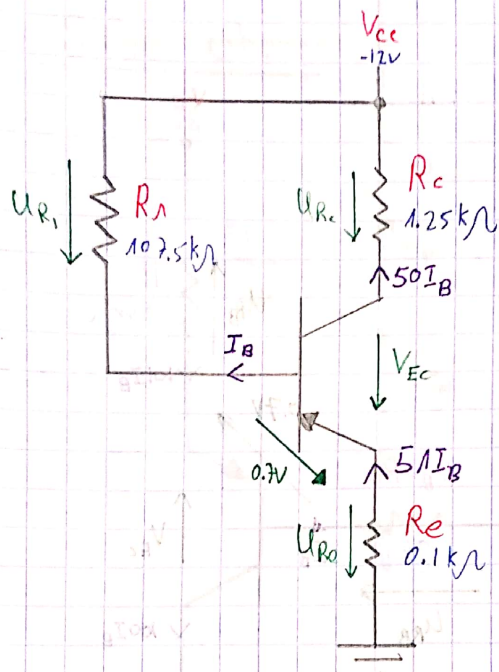

1C

10'1

$$V_{cc} - 0 = -U_{R1} - V_{EB} - U_{Re}$$

$$-12 = -107.5 I_B - 0.7 - 51 I_B \cdot 0.1$$

$$I_B = 100.355 \cdot 10^{-3} \text{ mA}$$

↓

$$I_c = 5.017 \text{ mA}$$

2'10

$$V_{cc} - 0 = -U_{Rc} - V_{EC} - U_{Re}$$

$$-12 = -50 I_B \cdot 1.25 - V_{EC} - 51 I_B \cdot 0.1$$

$$V_{EC} = 5.216 \text{ V}$$

$$V_{CE} = -6 \text{ V} / V_{EC} = 6 \text{ V} \quad \text{נקודת עבודה: } V_{CE} = 6 \text{ V}$$

$$V_{cc} - 0 = -U_{R1} - V_{EB} - U_{Re}$$

10'1

$$-12 = -R_1 \cdot I_B - 0.7 - 51 I_B \cdot 0.1$$

$$88.757 \cdot 10^{-3} (R_1 + 5.1) = 11.3$$

$$I_B (R_1 + 5.1) = 11.3$$

$$R_1 + 5.1 = 127.313$$

$$R_1 = 122.213 \text{ k}\Omega$$

2'10


$$V_{cc} - 0 = -U_{Rc} - V_{EC} - U_{Re}$$

$$-12 = -50 I_B \cdot 1.25 - 6 - 51 I_B \cdot 0.1$$


$$-6 = -62.5 I_B - 5.1 I_B$$

$$67.6 I_B = 6$$
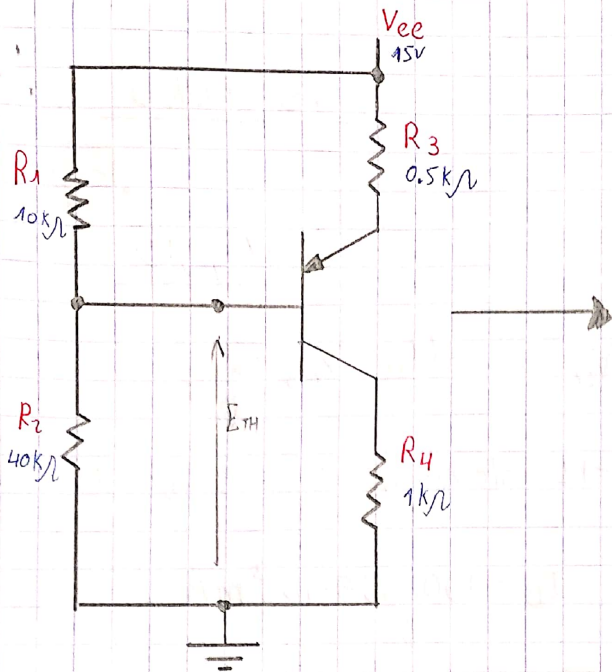
$$I_B = 88.757 \cdot 10^{-3} \text{ mA}$$



התנאים הם כדלקמן

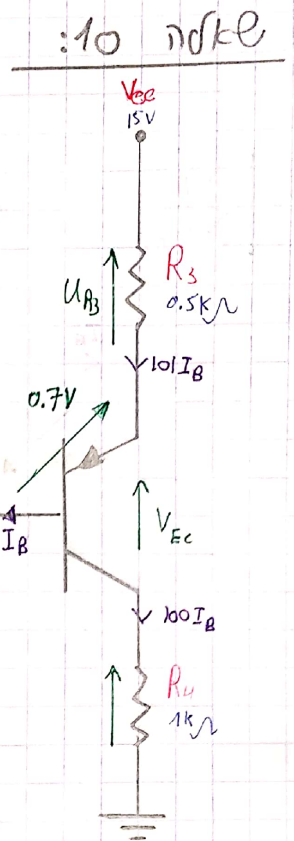

כאשר V_{BE} הוא הפוטנציאל בין הבסיס לאלמנט המוליך (P-N) ו- V_{BE} הוא הפוטנציאל בין הבסיס לאלמנט המוליך (P-N)

הנני מניח

הנני מניח

$$V_{cc} - 0 = U_{R3} + V_{EC} + U_{R4}$$

$$15 = 101I_B \cdot 0.5 + V_{EC} + 1 \cdot 100I_B$$

$$V_{EC} = 9.082V$$

$$V_{cc} - V_{TH} = U_{R3} + V_{EB} + U_{RB}$$

$$15 - 12 = 101I_B \cdot 0.5 + 0.7 + I_B \cdot 8$$

$$I_B = 39.316 \cdot 10^{-3} \text{ mA}$$

$$I_c = 3.931 \text{ mA}$$

הנני מניח R_1, R_2, R_3 הם כדלקמן I_B הוא הזרם הבסיסי R_4 הוא ההתנגדות של האלמנט המוליך (P-N)

$$11.783 = 15 \left(\frac{40}{40 + R_1} \right) + 49.833 \cdot 10^{-3} (40 || R_1)$$

$$11.783 = \frac{600}{40 + R_1} + 49.833 \cdot 10^{-3} \left(\frac{40 R_1}{40 + R_1} \right)$$

$$R_1 = 13.144 k\Omega$$

$$V_{cc} - V_{TH} = U_{R3} + V_{EB} + U_{RB}$$

$$15 - V_{TH} = 101I_B \cdot 0.5 + 0.7 + I_B \cdot R_{TH}$$

$$11.783 = V_{TH} + 49.833 \cdot 10^{-3} R_{TH}$$


$$11.783 = 15 \cdot \left(\frac{R_2}{R_1 + R_2} \right) + 49.833 \cdot 10^{-3} (R_1 || R_2)$$

$$V_{cc} - 0 = U_{R3} + V_{EC} + U_{R4}$$

$$15 = 101I_B \cdot 0.5 + 7.5 + 100I_B$$

$$7.5 = 150.5I_B$$
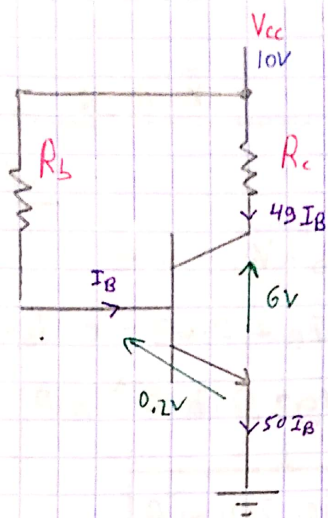
$$I_B = 49.833 \cdot 10^{-3} \text{ mA}$$



11. 10/10

$$I_C = 49 I_B = 5 \text{ mA}$$

$$I_B = 102.04 \cdot 10^{-3} \text{ mA}$$

:1 10/10

$$V_{CC} - 0 = U_{RB} + V_{BE}$$

$$10 = I_B \cdot R_B + 0.2$$

$$102.04 \cdot 10^{-3} R_B = 9.8$$

$$R_B = 96.04 \text{ k}\Omega$$


:2 10/10

$$V_{CC} - 0 = U_{RC} + V_{CE}$$

$$10 = I_C \cdot R_C + 6$$



$$4 = 5 R_C$$

$$R_C = 0.8 \text{ k}\Omega$$

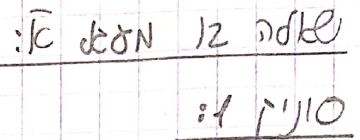

$$I_c = 19.201 \text{ mA}$$

$$V_{CE} = 4.52V$$

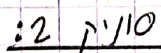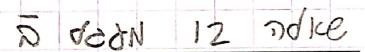


$$V_{CF} = 6.843V$$

$$I_c = 5.383 \text{ mA}$$

סוף 1:

Σ 028N 12 70/00

01 7'10

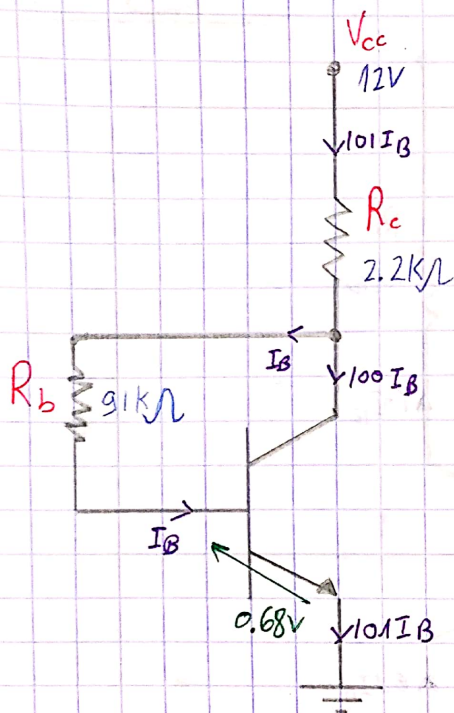

$$V_{cc} - 0 = U_{Rc} + U_{Rb} + V_{BE}$$

$$12 = 101 I_B \cdot 2.2 + I_B \cdot 91 + 0.68$$

$$I_B = 36.143 \cdot 10^{-3} \text{ mA}$$


$$I_C = 3.614 \text{ mA}$$

02 7'10

$$V_{cc} - 0 = U_{Rc} + V_{CE}$$

$$12 = 101 I_B \cdot 2.2 + V_{CE}$$

$$V_{CE} = 3.97 \text{ V}$$

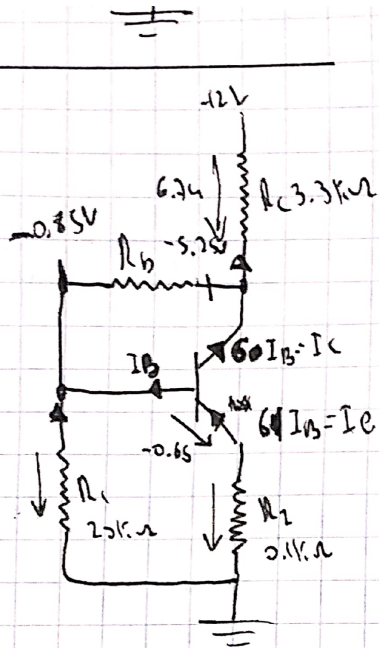

$$V_{R_2} = I_{R_2} \cdot R_2 = 2 \cdot 0.1 = 0.2 \text{ V}$$

$$\underline{U_{R_1}} = (V_{BE} + U_{R_2}) - 0 = 0.65 + 0.2 - 0 = \underline{0.85V}$$

$$I_{B2} = \frac{I_e}{\beta_1} = \frac{2}{61} = 32.786 \cdot 10^{-3} \text{ mA}$$



$$I_{R_b} = I_B + I_R = 42 \cdot 5 \cdot 10^{-3} + 32.786 \cdot 10^{-3} = \underline{75.286 \cdot 10^{-3} \text{ mA}}$$

$$\underline{I_{R_c}} = I_{R_b} + I_{R_c} = 75.286 \cdot 10^{-3} + 60.32.786 \cdot 10^{-3} = \underline{2.042 \text{ mA}}$$

$$\underline{U_{R2}} = I_{R1} \cdot R_2 = 2.042 \cdot 3.3 = \underline{6.74V}$$

$$\underline{U_{R_6}} = -0.75 - (-5.25) = \underline{4.5V}$$
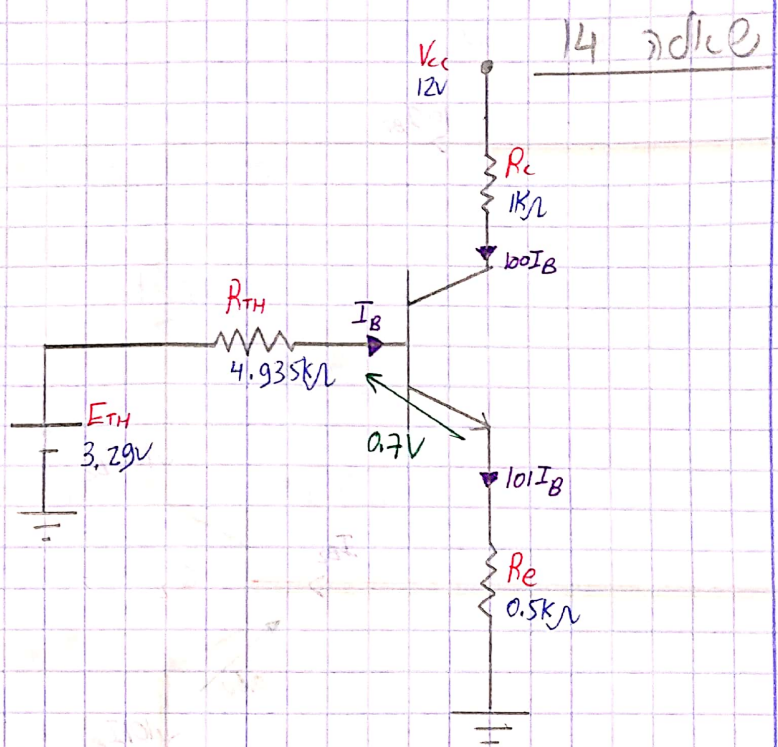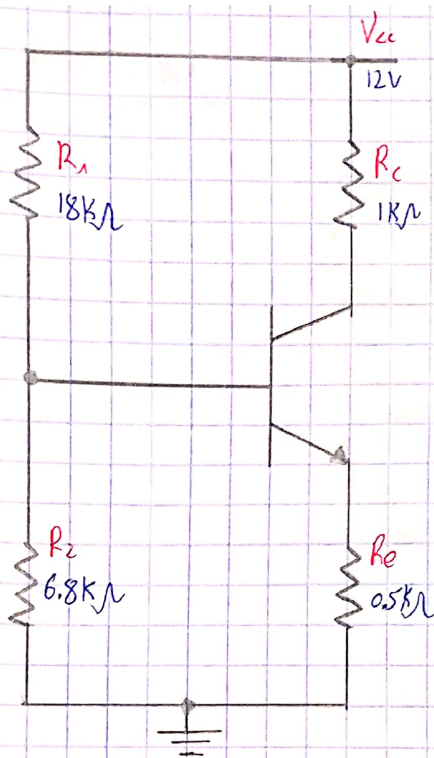
$$R_b = \frac{V_{Rb}}{I_{Rb}} = \frac{6.41}{75.231 \cdot 10^{-9}} = 58.5 \text{ k}\Omega$$



2.10

1.10

$$V_{CC} - 0 = U_{R_C} + V_{CE} + U_{R_E}$$

$$12 = 100 I_B \cdot 1 + V_{CE} + 101 I_B \cdot 0.5$$


$$V_{CE} = 4.967V$$

$$E_{TH} - 0 = U_{R_{TH}} + V_{BE} + U_{R_E}$$

$$3.29 = 4.935 I_B + 0.7 + 101 I_B \cdot 0.5$$

$$I_B = 46.726 \cdot 10^{-3} \text{ mA}$$

$$I_C = 4.672 \text{ mA}$$

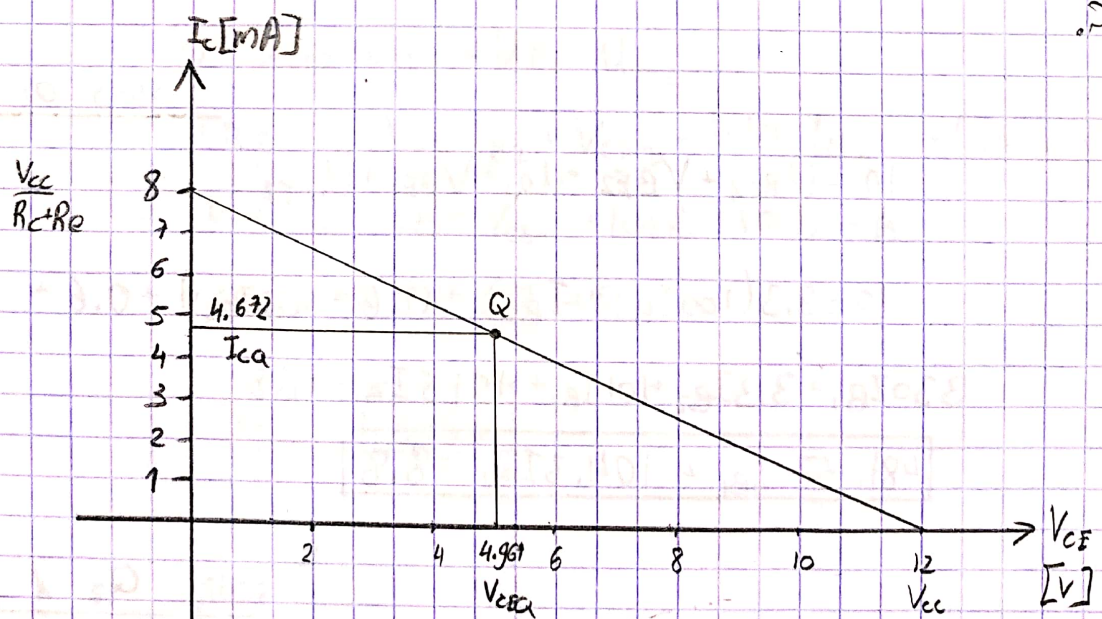

$$\begin{cases} 481.5 I_{B1} + 104.3 I_{B2} = 8.8 \\ 329 I_{B1} + 205.3 I_{B2} = 9.4 \end{cases}$$

$$I_{B1} = 12.802 \cdot 10^{-3} \text{ mA} \rightarrow [A]$$

$$I_{B2} = 25.270 \cdot 10^{-3} \text{ mA} \rightarrow [B]$$

↓

$$I_{C1} = 1.280 \text{ mA}$$

$$I_{C2} = 2.527 \text{ mA}$$

: Q1 p3 2 p110

$$10 = U_{RC1} + V_{CE1} + U_{RE1}$$

$$10 = 3.3(100 I_{B1} + I_{B2}) + V_{CE1} + 1.5 \cdot 101 I_{B1}$$

$$10 = 3.3(100A + B) + V_{CE1} + 1.5 \cdot 101 \cdot A$$

$$V_{CE1} = 10 - 330A - 3.3B - 151.5A$$

$$V_{CE1} = 10 - 481.5A - 3.3B$$

$$\boxed{V_{CE1} = 3.752 \text{ V}}$$

: Q2 p3 2 p110


$$10 = U_{RC2} + V_{CE2} + U_{R1} + U_{R2}$$

$$10 = 1.2 \cdot 100 I_{B2} + V_{CE2} + 1 \cdot 101 I_{B2} + 1 \cdot (101 I_{B2} - I_{B1})$$

$$10 = 1.2 \cdot 100B + V_{CE2} + 101B + 101B - A$$


$$V_{CE2} = 10 - 322B + A$$

$$\boxed{V_{CE2} = 1.875 \text{ V}}$$

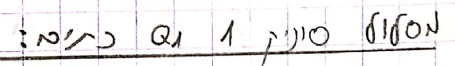

מסלול סיני 1 Q2 בחינה

$$329I_{B1} + 205.3I_{B2} = 9.4$$

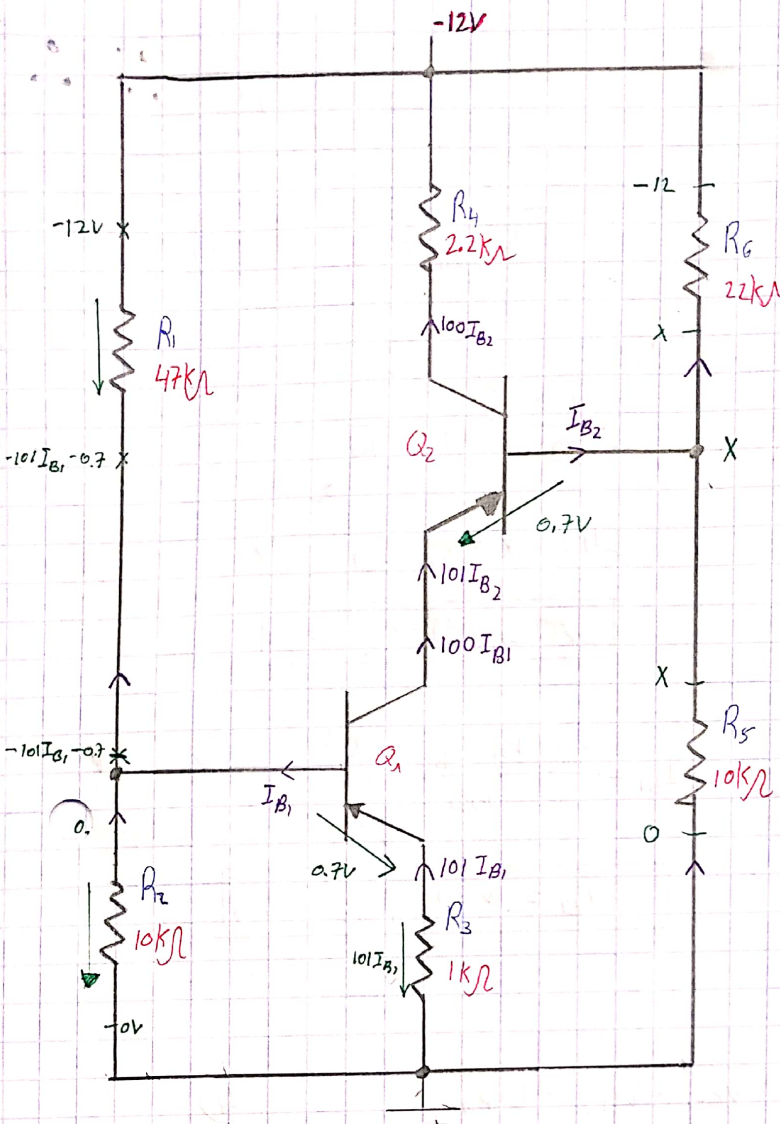

:48227

$$-U_{R2} = -U_{B3} - V_{EB}$$

$$U_{R2} = 101 I_{B1} + 0.7$$

$$I_{R1} = \frac{U_{R1}}{R_1} = \frac{-101 I_{B1} - 0.7 - (-12)}{47}$$

$$I_{R1} = \frac{11.3 - 101 I_{B1}}{47}$$

$$I_{R2} = \frac{U_{R2}}{R_2} = \frac{101 I_{B1} + 0.7}{10}$$

$$I_{B1} + I_{R2} = I_{R1}$$

$$I_{B1} + \frac{101 I_{B1} + 0.7}{10} = \frac{11.3 - 101 I_{B1}}{47}$$

$$I_{B1} = 12.863 \cdot 10^{-3} \text{ mA}$$

$$I_{R5} + I_{B2} = I_{R6}$$

$$\frac{-X}{10} + I_{B2} = \frac{X + 12}{22}$$

$$V_{B2} = X = -3.662 \text{ V}$$

$$(-12 - 0) = U_{R4} + V_{EC2} + V_{EC1} + U_{B3}$$

$$12 = 100 I_{B2} \cdot 2.2 + V_{EC2} + 1.663 + 101 I_{B1}$$

$$V_{EC2} = 6.236 \text{ V}$$

$$100 I_{B1} = 101 I_{B2}$$

$$I_{B2} = \frac{100 I_{B1}}{101} = 12.736 \cdot 10^{-3} \text{ mA}$$

$$0 - U_{R3} - V_{CE1} - V_{EB2} = X$$

$$0 - 101 I_{B1} - V_{EC1} - 0.7 = X$$

$$V_{EC1} = 1.663 \text{ V}$$

$$I_{C1} = 100 I_{B1} = 1.286 \text{ mA}$$


$$I_{C2} = 100 I_{B2} = 1.273 \text{ mA}$$

$$V_{B2} = -3.662 \text{ V}$$

$$V_{EC1} = 1.663 \text{ V}$$

$$V_{EC2} = 6.236 \text{ V}$$

:0'0'0

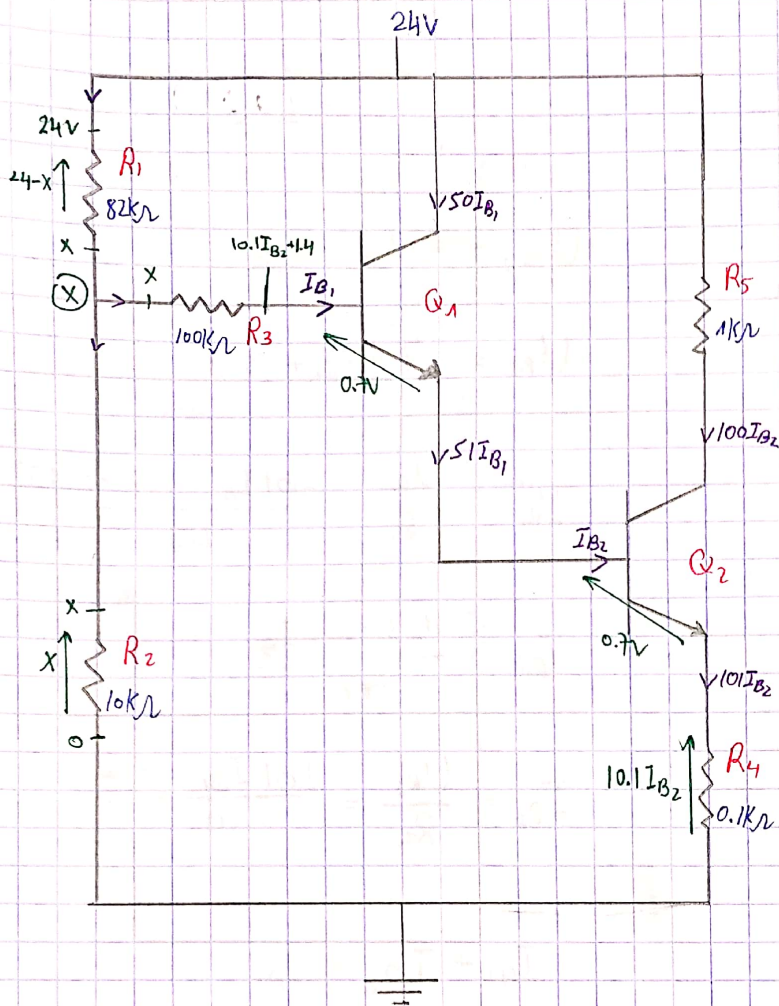

$$3 I_{B1} = I_{B2} \quad (1)$$

$$\frac{24-X}{82} = I_{B1} + \frac{X}{10} \quad (2)$$

$$240 - 10X = 820 I_{B1} + 82X$$

$$820 I_{B1} + 92X = 240$$

$$I_{B1} = \frac{X - (10.1 I_{B2} + 1.4)}{100} \quad (3)$$

$$100 I_{B1} = X - 10.1 I_{B2} - 1.4$$

$$24 - 0 = U_{R5} + V_{CE2} + U_{R4} \quad (5)$$

$$24 = 100 I_{B2} \cdot 1 + V_{CE2} + 10.1 I_{B2} \cdot 0.1$$

$$110.1 I_{B2} + V_{CE2} = 24$$

$$24 - 0 = V_{CE1} + V_{BE2} + U_{R4} \quad (4)$$

$$24 = V_{CE1} + 0.7 + 10.1 I_{B2} \cdot 0.1$$

$$V_{CE1} + 10.1 I_{B2} = 23.3$$

(3) (2) (1) נ'ען

$$\begin{cases} 820 I_{B1} + 92X = 240 \\ 615.1 I_{B1} - X = -1.4 \end{cases}$$

$$I_{B2} = 98.787 \cdot 10^{-3} \text{ mA}$$

$$I_{C2} = 9.878 \text{ mA}$$

$$I_{B1} = 1.937 \cdot 10^{-3} \text{ mA}$$

$$X = 2.591 \text{ V}$$

$$I_{C1} = 96.85 \cdot 10^{-3} \text{ mA}$$

(5) - נ'ען

$$110.1 I_{B2} + V_{CE2} = 24$$


$$V_{CE2} = 13.122 \text{ V}$$

(4) נ'ען

$$V_{CE1} + 10.1 I_{B2} = 23.3$$

$$V_{CE1} = 22.302 \text{ V}$$

תרגיל 4 מעגל

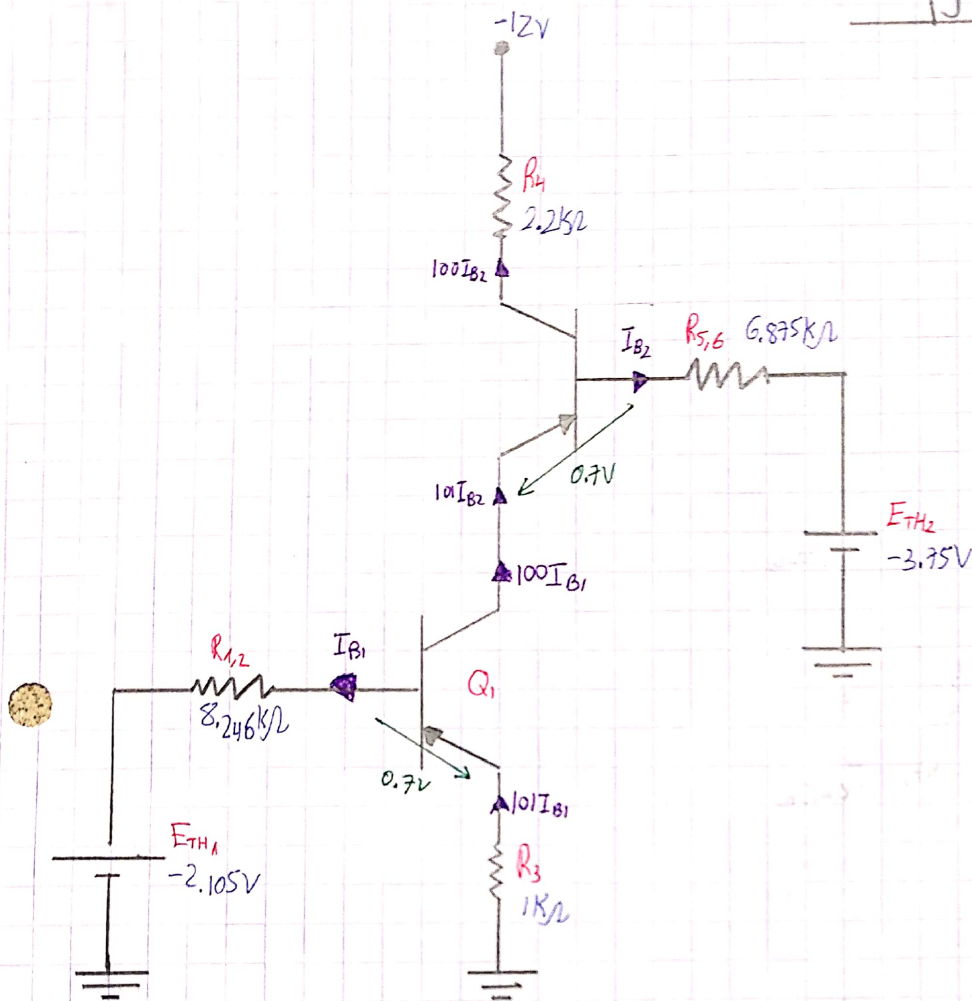

(Q1) 2 תנאים

$$\begin{aligned} 0 - E_{TH2} &= U_{R5,6} + V_{EB2} + V_{EC1} + U_{R3} \\ 3.75 &= 6.875 I_{B2} + 0.7 + V_{EC1} + 101 I_{B1} \end{aligned}$$

$$V_{EC1} = 1.663V$$

(Q2) 2 תנאים

$$\begin{aligned} 0 - (-12) &= U_{R4} + V_{EC2} + V_{EC1} + U_{R3} \\ 12 &= 100 I_{B2} \cdot 2.2 + V_{EC2} + 1.663 + 101 I_{B1} \end{aligned}$$

$$V_{EC2} = 6.236V$$

$$100 I_{B1} = 101 I_{B2}$$

$$I_{B2} = \frac{100}{101} I_{B1}$$

1 תנאי


$$\begin{aligned} 0 - E_{TH1} &= U_{R1,2} + V_{EB1} + U_{R3} \\ 2.105 &= 8.246 I_{B1} + 0.7 + 101 I_{B1} \end{aligned}$$

$$I_{B1} = 12.86 \cdot 10^{-3} \text{ mA}$$

$$I_{C1} = 100 I_{B1} = 1.286 \text{ mA}$$

$$I_{B2} = \frac{100}{101} I_{B1} = 12.733 \cdot 10^{-3} \text{ mA}$$

$$I_{C2} = 1.273 \text{ mA}$$

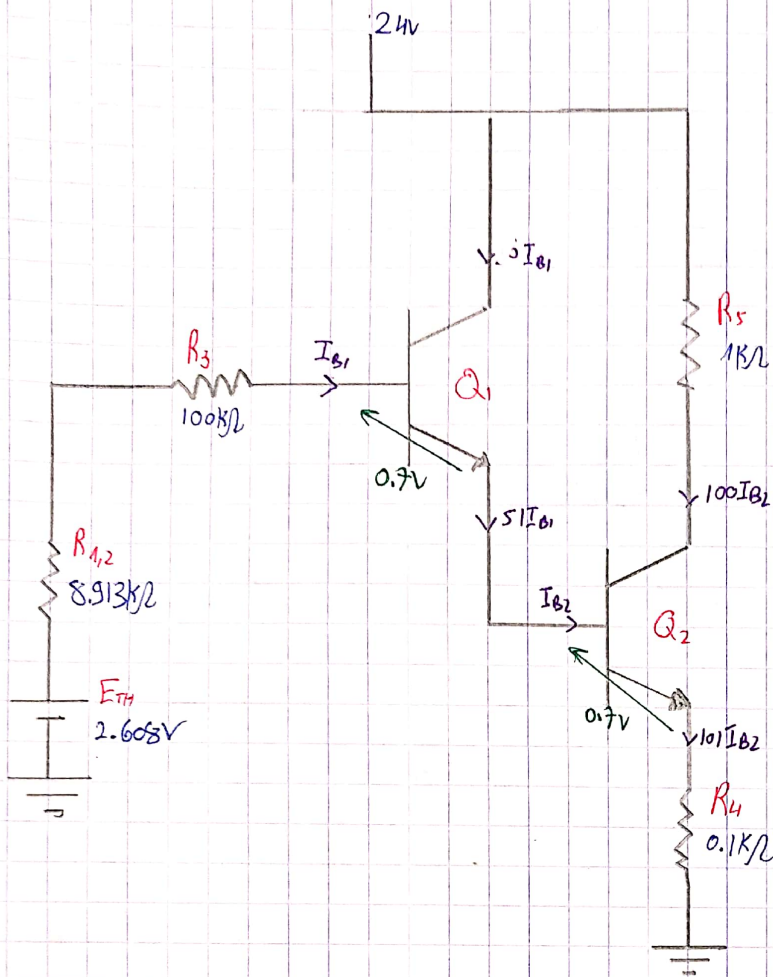

$$I_{B2} = 51 I_{B1}$$

22110

$$24 - 0 = V_{CE1} + V_{BE2} + U_{RH}$$

$$24 = V_{CE1} + 0.7 + 0.1 \cdot 101 I_{B2}$$

$$\boxed{V_{CE1} = 22.302V}$$

$$24 - 0 = U_{RS} + V_{CE2} + U_{RH}$$

$$24 = 100 I_{B2} \cdot 1 + V_{CE2} + 0.1 \cdot 101 I_{B2}$$

$$\boxed{V_{CE2} = 13.0123V}$$

12110

$$E_{TH} - 0 = U_{RA2} + U_{R3} + V_{BE1} + V_{BE2} + U_{RH}$$

$$2.608 = 8.913 I_{B1} + 100 I_{B1} + 0.7 + 0.7 + 0.1 I_{B2}$$

$$108.913 I_{B1} + 10.1 I_{B2} = 1.208$$

$$108.913 I_{B1} + 10.151 I_{B1} = 1.208$$


$$I_{B1} = 11.937 \cdot 10^{-3} \text{ mA}$$

$$I_{C1} = 50 I_{B1} = 96.848 \cdot 10^{-3} \text{ mA}$$

↓

$$I_{B2} = 51 I_{B1} = 98.785 \cdot 10^{-3} \text{ mA}$$
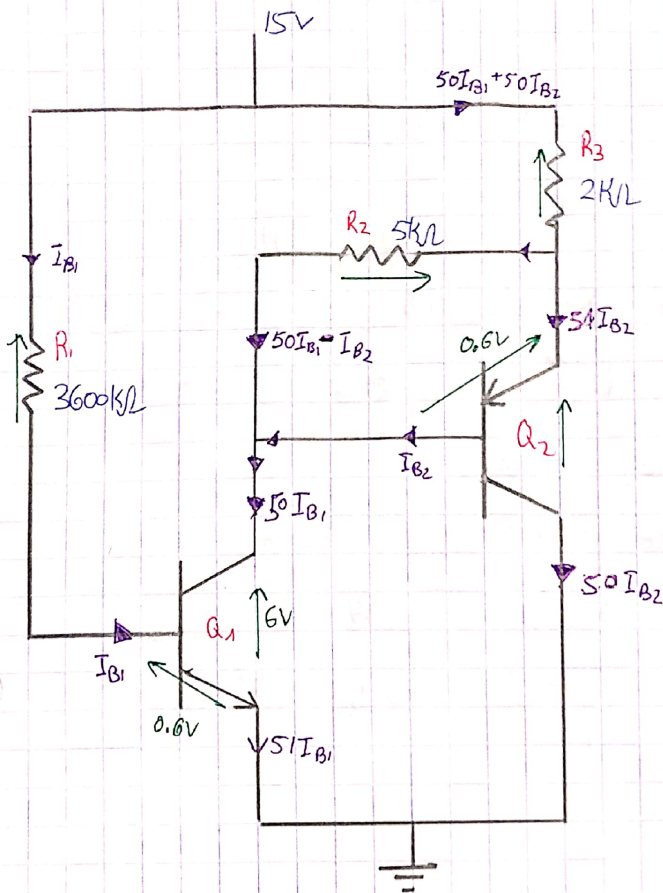
$$I_{C2} = 100 I_{B2} = 9.878 \text{ mA}$$



סניף 2 (Q1) / סניף 1 (Q2)

$$15 - 0 = U_{R3} + V_{EB2} + V_{CE1}$$

1k

$$15 - 0 = U_{R3} + U_{R2} + V_{CE1}$$

↓

$$U_{R2} = V_{EB2}$$

$$(50I_{B1} - I_{B2}) \cdot 5 = 0.6$$

$$I_{B2} = 80 \cdot 10^{-3} \text{ mA}$$

↓

$$I_{C2} = 4 \text{ mA}$$

$$15 - 0 = (50I_{B1} + 50I_{B2}) \cdot 2 + 0.6 + V_{CE1}$$

$$V_{CE1} = 6 \text{ V}$$

סניף 1 (Q1)

$$15 - 0 = U_{R1} + V_{BE1}$$

$$15 = 3600I_{B1} + 0.6$$

$$I_{B1} = 4 \cdot 10^{-3} \text{ mA}$$

↓

$$I_{C1} = 0.2 \text{ mA}$$

סניף 2 (Q2)

$$(15 - 0) = U_{R3} + V_{EC2}$$

1k

$$V_{EC2} = V_{CE1} + V_{EB2}$$

$$V_{EC2} = 6 + 0.6$$

$$V_{EC2} = 6.6 \text{ V}$$