

4

$$U_{RL} = 9V$$

$$I_{RL} = 790mA = 0.79A$$

$$E_1 = 1.5V$$

$$r_1 = 1.9\Omega$$


$$Q_1 = 0.3Ah$$

1202

$$R_L = \frac{U_{RL}}{I_{RL}} = \frac{9}{0.79} = 11.392\Omega$$

$$P_R = I_{RL}^2 \cdot R_L = 0.79^2 \cdot 11.392 = 7.109W \approx 7.11W$$
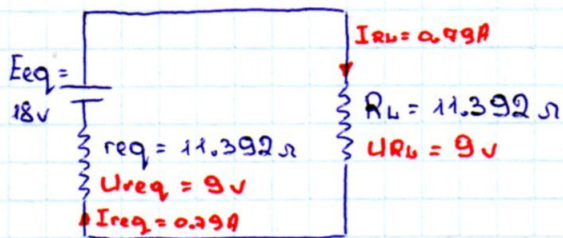
$$R_L = r_{eq} = 11.392\Omega \quad \text{при } \omega = 1000$$



$$\left. \begin{array}{l} R_L = r_{eq} \\ I_{RL} = I_{req} \end{array} \right\} \Rightarrow U_{RL} = U_{req} = 9V$$

$$\Downarrow$$

$$E_{eq} = U_{RL} + U_{req} = 9 + 9 = 18V$$

$$E_{eq} = E \cdot n$$

$$18 = 1.5n$$

$$n = 12$$

$$r_{eq} = \frac{n}{m} \cdot r$$

$$11.392 = \frac{22.8}{m}$$


$$11.392m = 22.8$$

$$m = 2.001 \approx 2$$

$$Q_{eq} = n \cdot Q$$

$$Q_{eq} = 2 \cdot 0.3 = 0.6 Ah$$
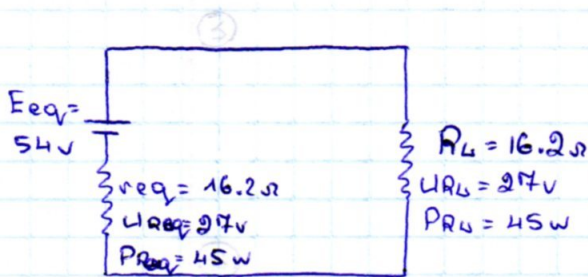
$$t = \frac{0.6}{0.79} = 0.759 h \cdot 60 = \boxed{45.54 \text{ min}}$$



WOB = 24 + 24 הכנסה ⑧

$\frac{1}{2} \cdot 100 = 50$ הכנסה

$E_1 = 3V$

$100 \cdot 0.02 = 2.0 \cdot E$ הכנסה $r_1 = 1.8\Omega$

$m = 2.18 = 0.2 \cdot 10.9$ הכנסה $Q_1 = 0.3Ah$

$U_{RL} = 27V$

$P_{RL} = 45W$

הכנסה

⑥

$$R_L = \frac{U_{RL}^2}{P_{RL}} = \frac{27^2}{45} = 16.2\Omega$$

$R_L = r_{eq}$ הכנסה

$$E_{eq} = U_{RL} + U_{req} = 27 + 27 = 54V$$

$$E_{eq} = E \cdot n$$

$$54 = 3n$$

$n = 18$


$$r_{eq} = \frac{n}{m} \cdot r$$

$$16.2 = \frac{18}{m} \cdot 1.8$$

$$16.2 = \frac{32.4}{m}$$

$$16.2m = 32.4$$

$m = 2$

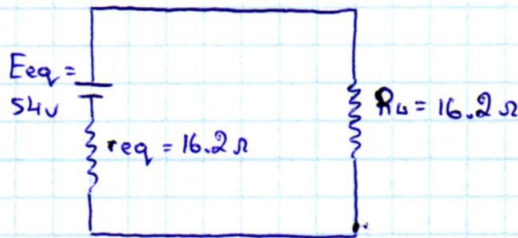

$$I_{eq} = \frac{E_{eq}}{R_L + r_{eq}} = \frac{54}{32.4} = 1.666\Omega \approx 1.67\Omega$$

$$U_{RL} = I_{eq} \cdot R_L = 1.67 \cdot 16.2 = \text{27V}$$

②

$$P_{eq} = P_{RL} + P_{req} = 45 + 45 = 90 \text{ W}$$


(1)

$$\eta_{RL} = \frac{45}{90} \cdot 100\% = \boxed{50\%}$$

$$Q_{eq} = m \cdot Q = 2 \cdot 0.3 = 0.6 \text{ Ah}$$

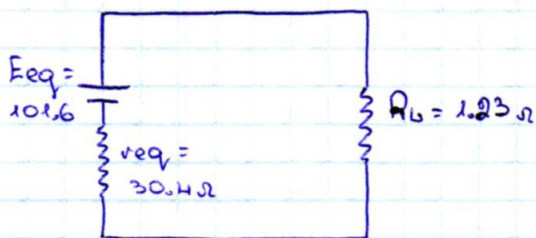(2)

$$t = \frac{Q_{eq}}{I_{eq}} = \frac{0.6}{1.67} = 0.359 \cdot 60 = \boxed{21.54 \text{ m}}$$



7

$$E_1 = 1.27V$$

$$r_1 = 0.38\Omega$$

$$Q_1 = 2.2Ah$$

$$R_L = 1.23\Omega$$

$$m = 1$$

$$n = 80$$

$$E_{eq} = n \cdot E = 80 \cdot 1.27 = 101.6V$$

$$r_{eq} = \frac{n}{m} \cdot r$$

$$r_{eq} = \frac{80}{1} \cdot 0.38 = 30.4\Omega$$

$$R_{eq} = R_L + r_{eq} = 1.23 + 30.4 = 31.63\Omega$$

$$I_{eq} = \frac{E_{eq}}{R_{eq}} = \frac{101.6}{31.63} = 3.212A$$

$$m = 80$$

$$n = 1$$

$$E_{eq} = n \cdot E = 1 \cdot 1.27 = 1.27V$$

$$r_{eq} = \frac{1}{80} \cdot 0.38 = 0.00475\Omega$$

$$R_{eq} = R_L + r_{eq} = 1.23 + 0.00475 = 1.23475\Omega$$

$$I_{eq} = \frac{E_{eq}}{R_{eq}} = \frac{1.27}{1.23475} = 1.028A$$

$$R_L = r_{eq} \leftarrow \text{when } m = n$$



$$E_1 = 1.27V$$

$$r_1 = 0.38\Omega$$

$$Q_1 = 2.2Ah$$

$$R_L = 1.23\Omega$$

$$m \cdot n = 80$$

$$\Downarrow$$

$$n = \frac{80}{m}$$

$$r_{eq} = \frac{n}{3} \cdot 0.38$$

$$1.23 = \frac{30}{3} \cdot 0.38$$

$$1.23 = \frac{80}{3} \cdot 0.38$$

$$1.23 = \frac{30.4}{m^2}$$

$$1.23 m^2 = 30.4$$

$$m = \pm \sqrt{24.715}$$

$$m_1 = 4.97 \approx 5$$

$$m_2 = -4.97 \leftarrow \text{negativ}$$

$$r_{eq} = \frac{n}{m} \cdot r$$

$$1.23 = \frac{n}{5} \cdot 0.38$$

$$1.23 = \frac{0.38n}{5}$$

$$6.15 = 0.38n$$


$$n = 16.18 \approx 16$$

$$E_{eq} = E \cdot n = 1.27 \cdot 16 = 20.32 \text{ V}$$

$$I_{eq} = \frac{E_{eq}}{r_{eq} + R_L} = \frac{20.32}{2.46} = 8.26 \text{ A}$$

$$Q_{eq} = m \cdot Q = 5 \cdot 2.2 = 11 \text{ Ah}$$
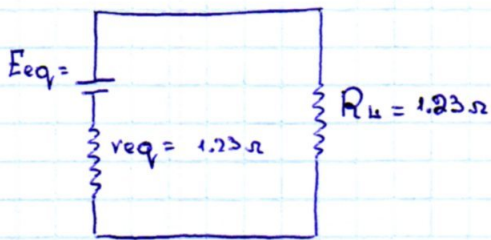
$$t = \frac{Q_{eq}}{I_{eq}} = \frac{11}{8.26} = 1.331 \text{ h} \cdot 60 \text{ min} = 79.86 \text{ min}$$



8

$$E_1 = 1.27V$$

$$r_1 = 0.38\Omega$$

$$Q_1 = 2.2Ah$$

$$R_L = 1.23$$

$$\left. \begin{matrix} K = n \\ L = m \end{matrix} \right\} n \cdot m = 80$$

8

8

$$n \cdot m = 80 \Rightarrow m = \frac{80}{n}$$

$$req = \frac{80}{n} \cdot 0.38 = \frac{80}{n^2} \cdot 0.38 = \frac{30.4}{n^2}$$

$$req = R_L = 1.23\Omega$$

$$1.23 = \frac{30.4}{n^2}$$

$$1.23n^2 = 30.4$$

$$n^2 = 24.715$$

$$n = \pm \sqrt{24.715} = \begin{cases} +4.971 \approx 5 \\ -4.971 \leftarrow \text{מחזורי}$$

$$n = 5$$

$$req = \frac{n}{m} \cdot 0.38 = \frac{n}{5} \cdot 0.38 = \frac{0.38n}{5}$$


$$1.23\Omega = \frac{0.38n}{5}$$

$$6.15 = 0.38n$$

$$n = 16.184 \approx 16$$

$$n = 16$$

8

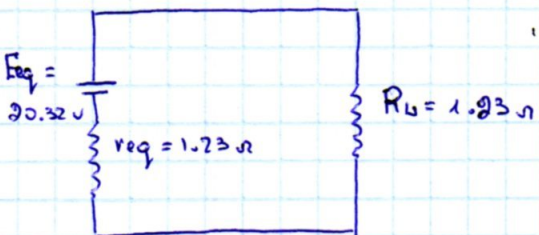

$$n = 16$$

$$m = 5$$

$$E_1 = 1.27V$$

$$r_1 = 0.38\Omega$$

$$Q_1 = 2.2Ah$$

$$E_{eq} = 8 n \cdot E_1 = 16 \cdot 1.27 = 20.32 \text{ V}$$


$$I_{eq} = \frac{E_{eq}}{r_{eq} + R_L} = \frac{20.32}{2.46} = 8.26 \text{ A}$$

$$U_{R_L} = I_{eq} \cdot R_L = 8.26 \cdot 1.23 = 10.1598 \text{ V}$$

$$P_{R_L} = I_{eq}^2 \cdot R_L = 8.26^2 \cdot 1.23 = 83.919 \text{ W}$$

$$Q_{eq} = m \cdot Q_1 = 5 \cdot 2.2 = 11 \text{ Ah}$$
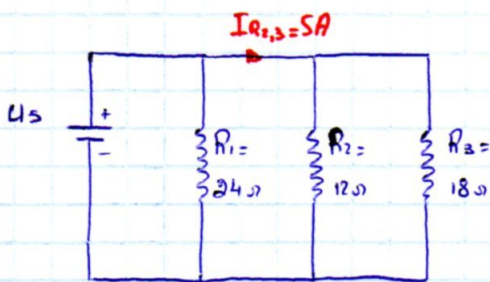
$$t = \frac{Q_{eq}}{I_{eq}} = \frac{11}{8.26} = 1.33 \text{ h} \cdot 60 \text{ min} = 79.8 \text{ min}$$



၁၂၅၅

$$R_{2,3} = R_2 \parallel R_3 = \frac{12 \cdot 18}{12 + 18} = 7.2\ \Omega$$

$$I_{R2,3} = I_T \frac{R_1}{R_1 + R_{2,3}}$$

$$5 = I_T \frac{24}{24 + 7.2}$$

$$5 = \frac{24 I_T}{31.2}$$

$$156 = 24 I_T$$

$$I_T = 6.5\text{ A}$$

$$I_{R1} = I_T - I_{R2,3} = 6.5 - 5 = 1.5\text{ A}$$

$$U_{R1} = I_{R1} \cdot R_1 = 1.5 \cdot 24 = 36\text{ V}$$

$$I_{R2} = I_{R2,3} \frac{R_3}{R_2 + R_3}$$

$$I_{R2} = 5 \frac{18}{18 + 12} = 5 \frac{18}{30} = 3\text{ A}$$

$$I_{R3} = I_{R2,3} - I_{R2} = 5 - 3 = 2\text{ A}$$


၁၂၅၅

$$I_{R1} = 1.5\text{ A}$$

$$I_{R2} = 3\text{ A}$$


$$I_{R3} = 2\text{ A}$$

$$U_s = 36\text{ V}$$

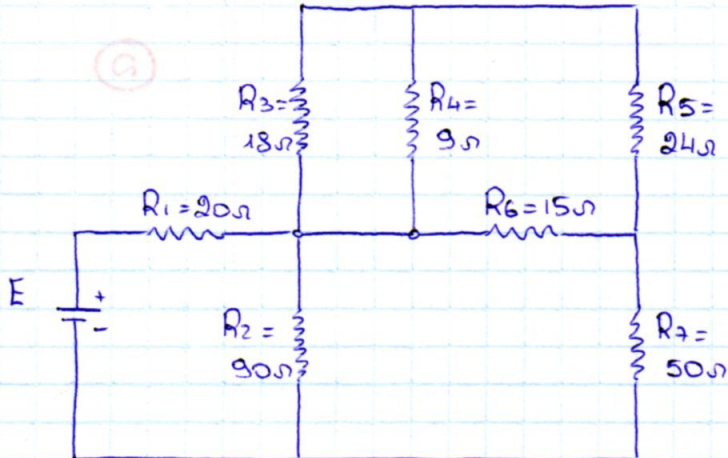


③
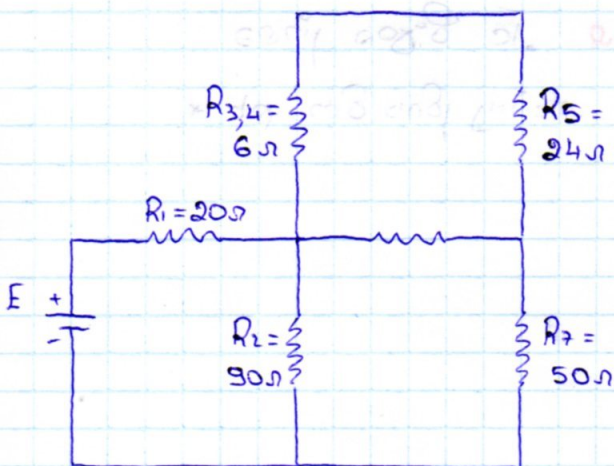
$$R_{3,4} = R_3 \parallel R_4 = \frac{18 \cdot 9}{18 + 9} = 6\Omega$$



$$R_{3-5} = R_{3,4} + R_5 = 6 + 24 = 30\Omega$$

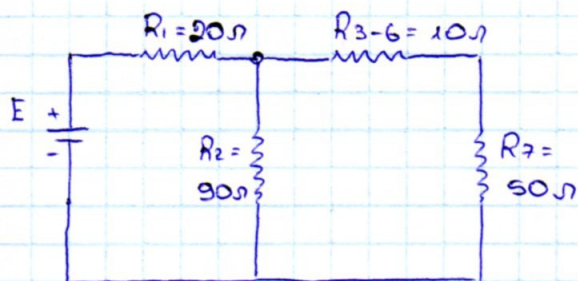
$$R_{3-6} = R_{3-5} \parallel R_6 = \frac{30 \cdot 15}{30 + 15} = 10\Omega$$



$$R_{3-7} = R_{3-6} + R_7 = 10 + 50 = 60\Omega$$

$$R_{2-7} = R_2 \parallel R_{3-7} = \frac{90 \cdot 60}{90 + 60} = 36\Omega$$
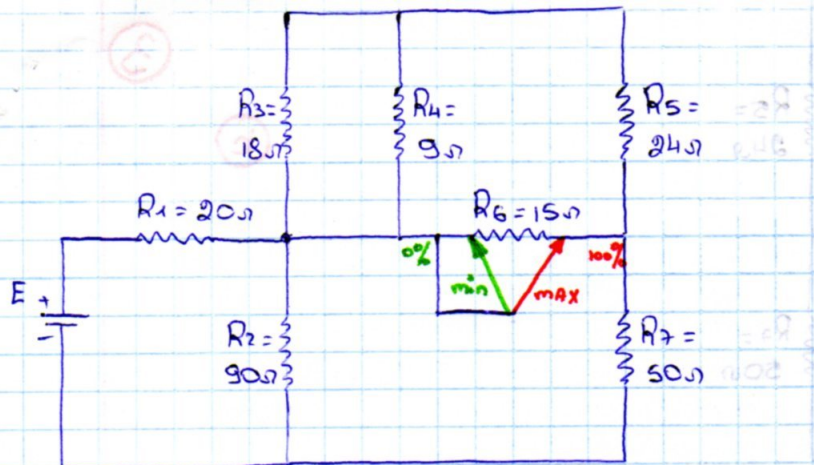
$$R_T = R_1 + R_{2-7} = 20 + 36 = \boxed{56\Omega}$$




פתרון

• כדי למצוא את המינימום והמקסימום של ההתנגדות הכוללת *

$R_T = 56\Omega = R_{Tmax} = 56\Omega$ • כל ההתנגדות

• כל ההתנגדות הכוללת

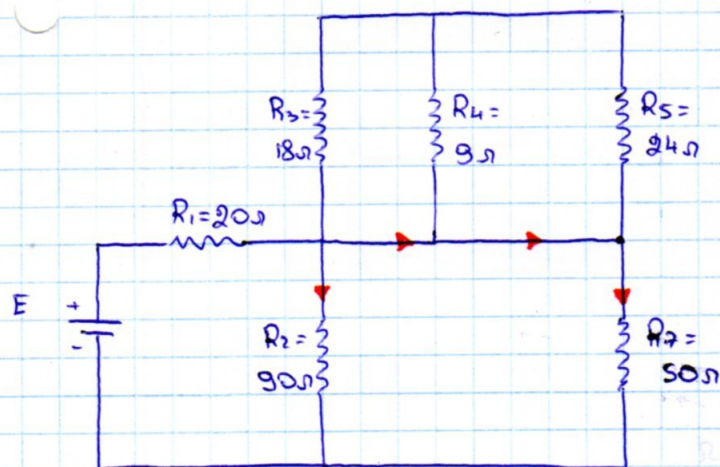

$$R_{2,7} = R_2 \parallel R_7 = \frac{90 \cdot 50}{90 + 50} = 32.142\Omega$$

$$R_T = R_1 + R_{2,7} = 20 + 32.142 = 52.142\Omega$$

$$R_{Tmin} = 52.142\Omega$$